

GS5581 Application Note

Typical Application Circuit

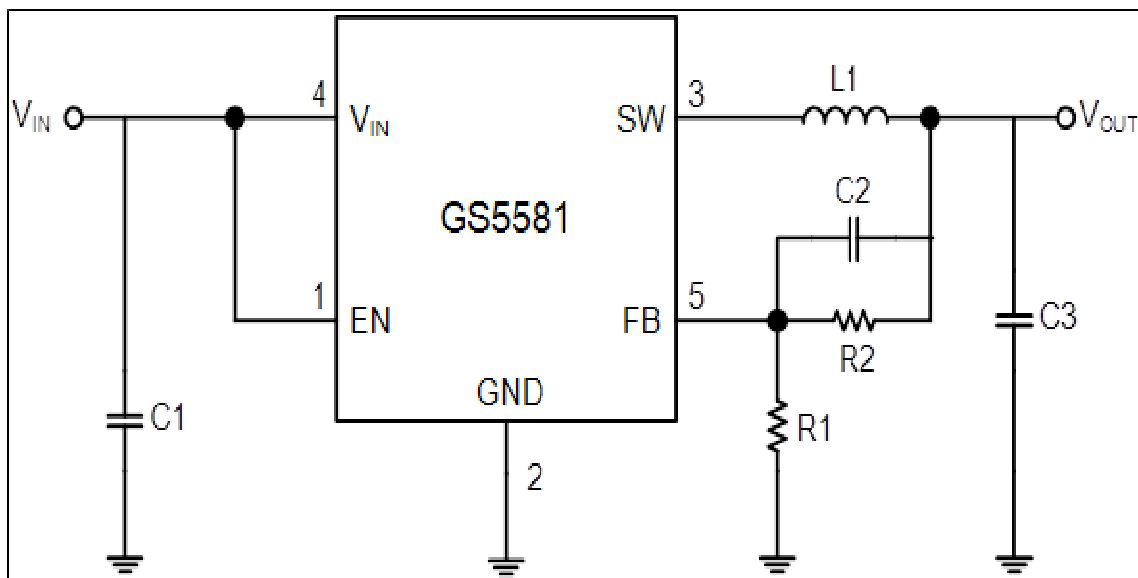


Table 1 recommended Component Selection

V _{OUT}	R ₂	R ₁	C ₂	L ₁	C ₁	C ₃
3.3V	540K	120K	20~220pF	4.7 μH	22 μF	22 μF
2.5V	380K	120K	20~220pF	4.7 μH	22 μF	22 μF
1.8V	200K	100K	20~220pF	2.2 μH	22 μF	22 μF
1.5V	150K	100K	20~220pF	2.2 μH	22 μF	22 μF
1.2V	100K	100K	20~220pF	2.2 μH	22 μF	22 μF
1.0V	100K	150K	20~220pF	2.2 μH	22 μF	22 μF

Setting the Output Voltage

The internal reference V_{REF} is 0.6V(Typical).The output voltage is divided by a resistor,R1 and R2 to the FB pin. The output voltage is given by:

$$V_{OUT}=0.6V \times \left(1 + \frac{R_2}{R_1}\right)$$

Globaltech (Asia) Semiconductor Co., Ltd.

4F.,No.43-1,Lane 11,Sec.6,Minquan E.Rd,Neihu District,Taipei City 114,Taiwan
Tel:886-2-26579980 Fax:886-2-26573630

Inductor Selection

For most designs, the GS5581 operates with inductors of 1 μ H to 4.7 μ H. Low inductance values are physically smaller but require faster switching, which results in some efficiency loss. The inductor value can be derived from the following equation:

$$L = \frac{V_{OUT} \times (V_{IN} - V_{OUT})}{V_{IN} \times \Delta I_L \times f_{OSC}}$$

Where ΔI_L is inductor Ripple Current. Large value inductors result in lower ripple current and small value inductors result in high ripple current. For optimum voltage-positioning load transients, choose an inductor with DC series resistance in the 50m Ω to 150m Ω range.

Input Capacitor Selection

With the maximum load current at 1.0A, the maximum ripple current through input capacitor is about 0.6Arms. A typical X7R or better grade ceramic capacitor with 6V rating and greater than 10 μ F capacitance can handle this ripple current well. To minimize the potential noise problem, place this ceramic capacitor really close to the IN and

GND pins. Care should be taken to minimize the loop area formed by C_{IN}, and IN/GND pins.

Output Capacitor Selection

The output capacitor is required to keep the output voltage ripple small and to ensure regulation loop stability. The output capacitor must have low impedance at the switching frequency. Ceramic capacitors with X5R or X7R dielectrics are recommended due to their low ESR and high ripple current ratings.

The output ripple ΔV_{OUT} is determined by:

$$\Delta V_{OUT} \leq \frac{V_{OUT} \times (V_{IN} - V_{OUT})}{V_{IN} \times f_{OSC} \times L} \times \left(ESR + \frac{1}{8 \times f_{OSC} \times C3} \right)$$

A 10 μ F ceramic Capacitor can satisfy most applications.

PC Board Layout Checklist


When laying out the printed circuit board, the following checking should be used to ensure proper operation of the GS5581. Check the following in your layout:

1. The power traces, consisting of the GND trace, the SW trace and the V_{IN} trace should be kept short, direct and wide.
2. Does the (+) plates of C_{IN} connect to V_{IN} as closely as possible.
This capacitor provides the AC current to the internal power MOSFET.
3. Keep the switching node, SW, away from the sensitive V_{OUT} node.
4. Keep the (-) plates of C_{IN} and C_{OUT} as close as possible.

Globaltech (Asia) Semiconductor Co., Ltd.

4F.,No.43-1,Lane 11,Sec.6,Minquan E.Rd,Neihu District,Taipei City 114,Taiwan
Tel:886-2-26579980 Fax:886-2-26573630

Top Layout

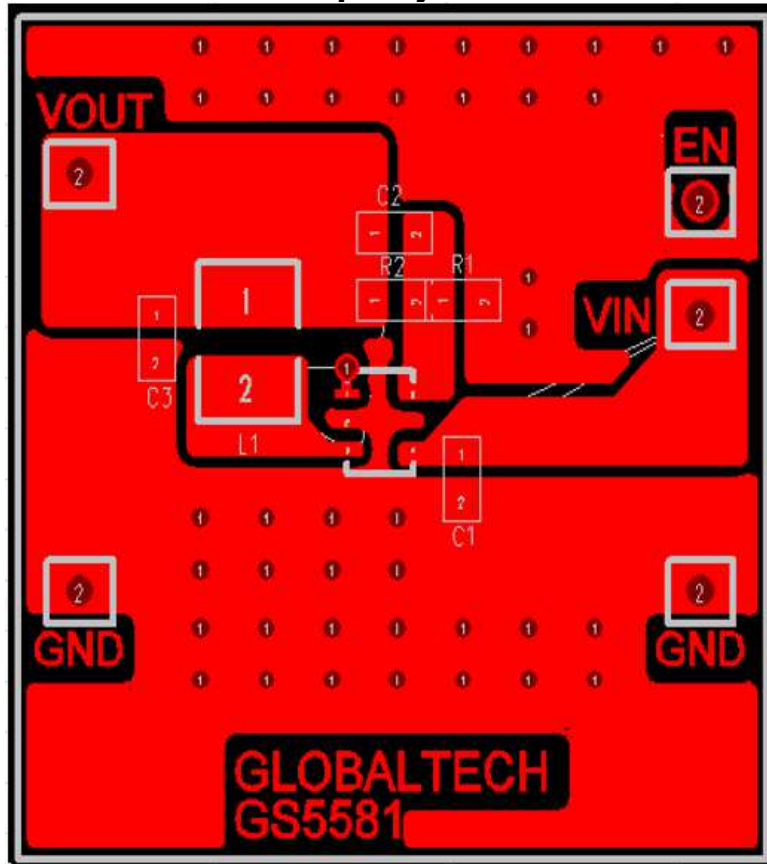

Bottom Layout

